

TI Designs: PMP9755 Reference Guide

Backup Power Solution Using Supercap with TPS61030 for Data Concentrator Circuit



TI Designs

TI Designs are analog solutions created by TI's analog experts. Reference designs offer the theory, component selection, and simulation of useful circuits. Circuit modifications that help to meet alternate design goals are also discussed.

Circuit Description

This reference design delivers a backup power circuits using a supercap with the boost converter TPS61030. In the low-power system that requires a backup switchover circuit at system's failure, a supercap together with TPS61030 could provide sufficient power to maintain data communication prior to the whole system's complete shutdown.



Design Resources

[Design Page](#)
[TPS61030](#)
[TL321A](#)

All Design files
 Product Folder
 Product Folder



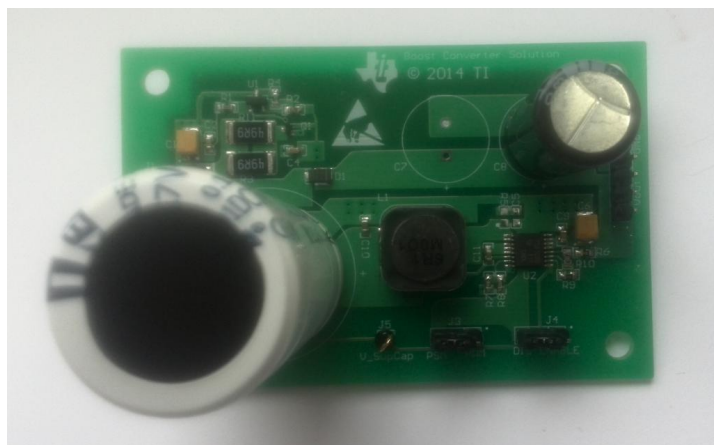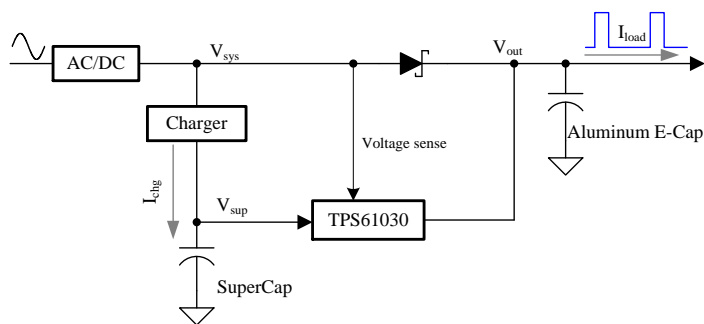[Ask The Analog Experts](#)
[WEBENCH® Design Center](#)
[TI Precision Designs Library](#)



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

TINA-TI is a trademark of Texas Instruments
 WEBENCH is a registered trademark of Texas Instruments

1 Introduction

Data concentrator is a critical device in automated metering infrastructure of smart grid. It securely aggregates the data from a number of meters and sends the data to the centralized utility servers via GPRS, GSM or other telecom networks. The data concentrator must operate for a period of time in case of the power supply failure or system brownout, which requires sufficient backup power for the equipment to the data storage or communication. So an additional energy storage device is applied in the data concentrator, either the battery or supercap. Battery has higher energy density while the supercap has better performance at output inrush current capability and lifetime which makes the supercap more competitive for the application in the data concentrator.

As the output voltage of one cell supercap is not higher than 2.7V, a boost converter is needed to raise the output voltage to power the GSM/GPRS module, the voltage of which is higher than 3.6V normally. Furthermore, the low input voltage boost converter can fully utilize the supercap's energy.

This reference design illustrates a backup power solution for the data concentrator using the boost converter TPS61030 and a supercap. The design includes the schematic and layout design, components selection and performance waveforms.

2 Design Process

2.1 Block Diagram and Operating Principle

Figure 1 shows the block diagram of the reference design. It mainly consists of a supercap, a charger circuit for supercap, and a boost converter.

Normally, the V_{sys} is powered by the grid and the voltage can be set to 5.3V, using device such as an adaptor. The output voltage V_{out} is around 5V considering 0.3V forward voltage of the schottky diode. At the meantime, the boost converter TPS61030 stops switching and the V_{sys} charges the supercap if its voltage V_{sup} is lower than 2.65V

If the grid browns out and V_{sys} drops down to lower than 5V, TPS61030 starts switching and maintains V_{out} at 5V utilizing the energy of supercap. The schottky diode prevents the current flow from V_{out} to V_{sys} .

Figure 2 shows the theoretical operating waveforms of this reference design. The main load I_{load} is a GPRS class 10 module, of which the average current is about 500mA. But the pulse current of I_{load} reaches 2A and lasts 1.154ms. In order to deal with the pulse current, aluminum electrolytic capacitors are applied at output to support V_{out} during 1.154ms period. Using this aluminum E-capacitor, the output current requirement for the adaptor and boost converter is reduced to 500mA, which will also reduce the cost of the system.

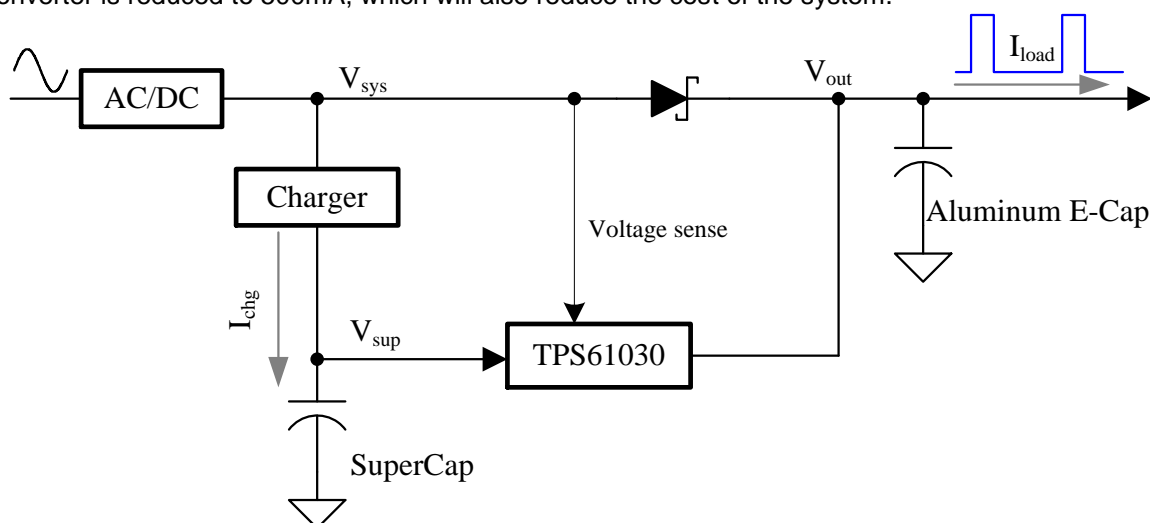


Figure 1: Reference Design Block Diagram

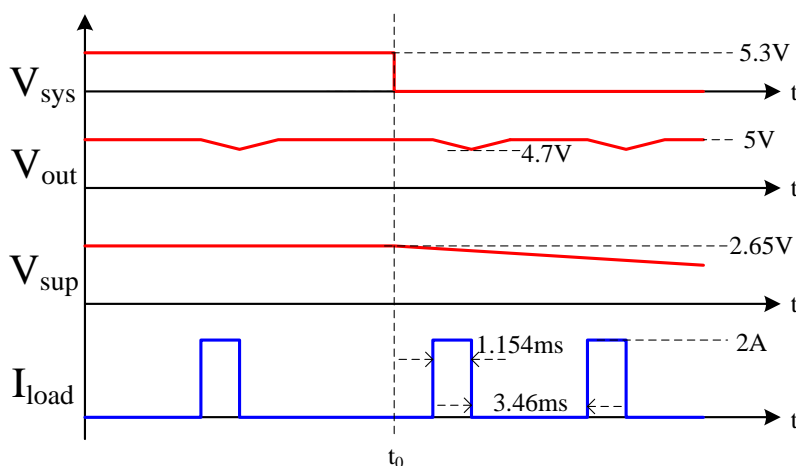


Figure 2: Reference Design Operating Waveform

In order to stop the TPS61030 from switching at the V_{sys} power on condition, the boost converter TPS61030 must adjust its regulation voltage to a point lower than the V_{out} . This function is implemented by TPS61030 LBI pin and LBO pin (pin 6 and pin 7). When $V_{sys}=5.3V$, the voltage of LBI is defined by the divider resistors in Figure 4.

$$V_{LBI} = \frac{R_7}{R_7 + R_8} \cdot V_{SYS} = \frac{100}{100 + 909} \times 5.3 \approx 525 mV$$

As the V_{LBI} is higher than 510mV, the LBO pin will be high impedance, and the TPS61030 regulation voltage V_{out_re} is defined by equation (3), where R_6 and R_{10} are the feedback divide resistors, and the V_{ref} is the reference voltage for FB pin.

$$V_{out_re} = \frac{R_6 + R_{I0}}{R_{I0}} \cdot V_{ref} = \frac{1000+124}{124} \times 0.5 \approx 4.5V \quad (3)$$

As the real $V_{out}=5V$, V_{out_re} can be set to 4.5V, which is lower than real V_{out} even considering the voltage drop caused by load transient. The V_{out_re} at this condition should be not too low; otherwise the high power dissipation may occur at the feedback resistor. At the same time, the power save mode of TPS61030 must be enable (SYNC PIN connect to GND) to stop the TPS61030 from switching. The boost converter only consumes quiescent current, 20 μA typically.

When the V_{sys} powers off, and becomes lower than 5V, the V_{LBI} will be lower than 510mV. An internal MOSFET shorts the LBO pin to GND, thus V_{out_re} will be

$$V_{out_re} = \frac{R_6 + R_{10} // R_9}{R_{10} // R_9} \cdot V_{ref} = \frac{1000 + 124 // 1000}{124 // 1000} \times 0.5 \approx 5.0V$$

The TPS61030 starts operating and maintains the $V_{out} = V_{out_re} = 5V$. As $V_{out} > V_{sys}$, the Schottky diode D1 prevents reverse current flowing from V_{out} to V_{sys} .

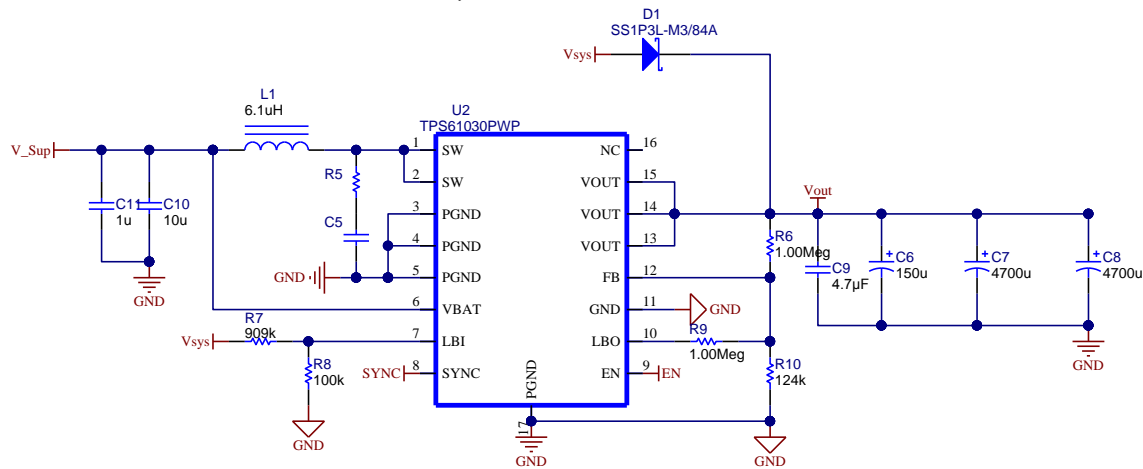


Figure 4: Boost Converter Circuit

As in Figure 2, the main load is the GPRS class 10 module with an average output current around 500mA. The capacity of the supercap is defined by equation (4), obtained from energy conversation principle.

$$\frac{C_{\text{sup}}}{2} (V_{\text{sup_max}}^2 - V_{\text{sup_min}}^2) = \frac{V_{\text{out}} \cdot I_{\text{out}}}{\eta} \cdot T \quad (4)$$

Where

V_{sup_max} : maximum voltage of the supercap;

$V_{sup\ min}$: minimum voltage of the supercap, defined by the UVLO of the TPS61030;

η : efficiency of the TPS61030; T : operating period after V_{SYS} power off;

Giving $V_{sup_max} = 2.65V$, $V_{sup_min} = 1.7V$, $\eta = 75\%$, $T = 60s$, the C_{sup} is

$$C_{\text{sup}} = \frac{2 \times 5 \times 0.5}{0.75 \times (2.65 \times 2.65 - 1.75 \times 1.75)} \cdot 60 = 97 \text{ Farad}$$

A 100Farad/2.7V supercap is selected in the reference design.

The inductor peak current of TPS61030 is defined by the equation (5) from its datasheet, where L is the input inductor, and f_s is the switching frequency. The TPS61030 limits its inductor peak current at typical 4A, so the maximum output current is defined by equation (6).

$$I_{L_peak} = \frac{V_{out} \cdot I_{out}}{V_{in} \cdot \eta} + \frac{1}{2} \frac{(V_{out} - V_{in}) \cdot V_{in}}{L \cdot V_{out} \cdot f_s} \quad (5)$$

$$I_{out} = \frac{V_{in} \cdot \eta}{V_{out}} \left[I_{L_peak} - \frac{1}{2} \frac{(V_{out} - V_{in}) \cdot V_{in}}{L \cdot V_{out} \cdot f_s} \right] \quad (6)$$

In the reference design, $L = 6.1\mu\text{H}$, and $f_s = 600\text{kHz}$ according to the TPS61030 datasheet. The maximum output current at $V_{in}=1.7\text{V}$ is the smallest, which is

$$I_{\max_1.7} = \frac{1.7 \times 0.75}{5} \times \left[4 - \frac{1}{2} \frac{(5-1.7) \times 1.7}{6.1\mu \times 5 \times 600k} \right] \approx 0.98\text{A}$$

This maximum output current at $V_{in} = 1.7\text{V}$ is higher than the average load current 500mA, but smaller than the peak current 2A. So an aluminum electrolytic capacitor is added at the output to support current gap during this 1.154ms period. The V_{out} drop can be calculated by equation (7), where C_{alu} and ESR_{alu} are the capacitance and effect series resistor of the aluminum electrolytic capacitor respectively.

$$\Delta V_{alu} = \frac{I_{load_peak} - I_{\max_1.7}}{C_{alu}} \cdot 1.154\text{ms} + (I_{load_peak} - I_{\max_1.7}) \cdot ESR_{alu} \quad (7)$$

A 4700μF capacitor EEUFR0J472 is adopted in the reference design. Its ESR is 15mΩ at 20°C. According to the equation (7), the voltage drop of the V_{out} is

$$\Delta V_{alu} = \frac{2\text{A} - 0.98\text{A}}{4700\mu\text{F}} \times 1.154\text{ms} + (2\text{A} - 0.98\text{A}) \times 15\text{m}\Omega \approx 265\text{mV}$$

So the minimum output voltage of V_{out} is about 4.74V, which is high enough to support the GPRS module.

Although a large aluminum electrolytic capacitor is used, A small ceramic capacitor combined with a tantalum capacitor or a ceramic capacitor larger than 47μF is still needed to absorb the switching current of the inductor, because ESL (Effective Series Inductor) of an aluminum capacitor make it not suitable to smooth high frequency voltage ripple. The small ceramic capacitor combined with a tantalum capacitor is adopted at this reference design.

2.3 PCB Layout

The reference design is implemented using 7.8cm by 5cm and 2 layers PCB. Figure 5 shows the top layer and top silk screen. All the components are placed in top layer. The C3 is the 100F/2.7V supercap. The C7 and C8 are the output aluminum capacitors. The charger circuit is placed in upper left corner of the PCB, while boost converter with its external component is placed at the bottom right. Make sure the output ceramic capacitor is as close as possible to the TPS61030.

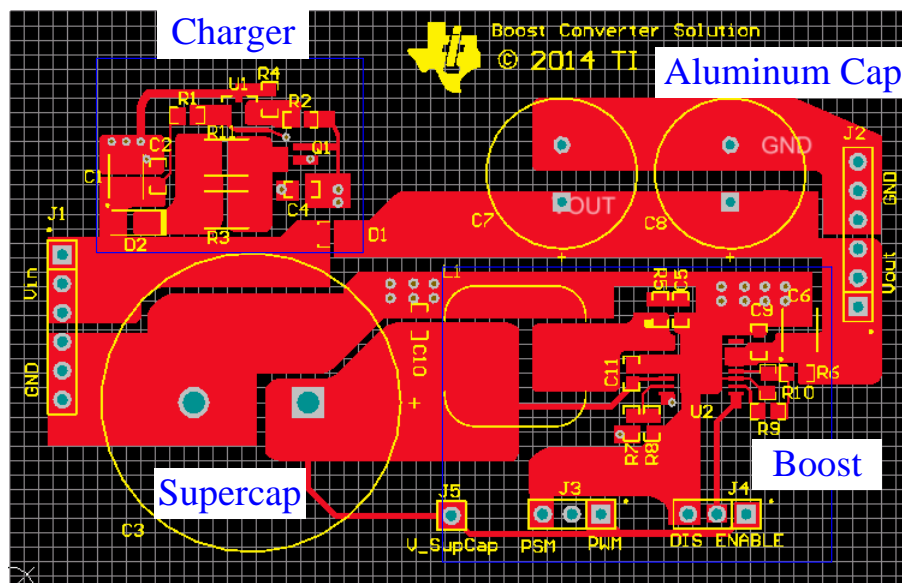


Figure 5: Top Layer and Top Silkscreen

The Figure 6 shows the layout of bottom layer.

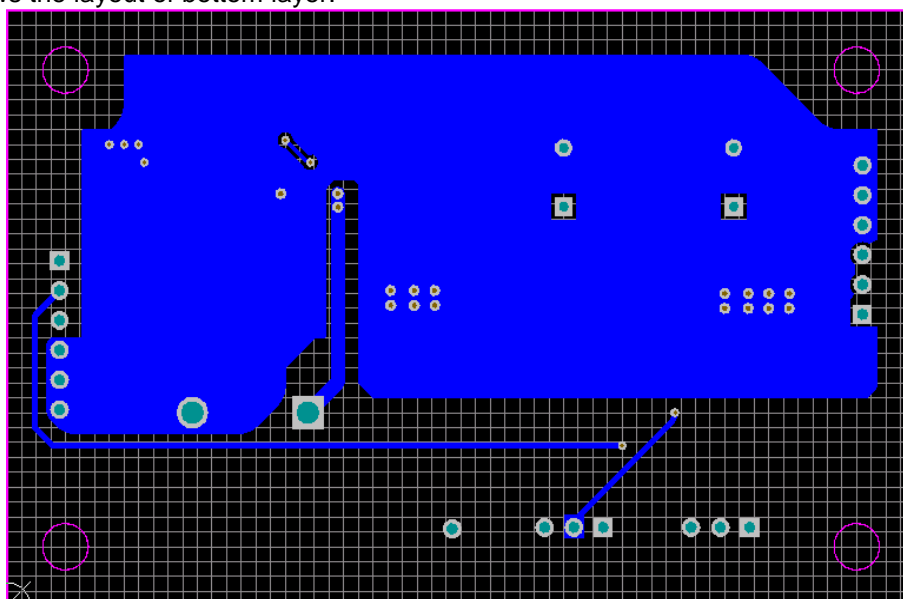


Figure 6: Bottom Layer

The final reference design board is shown in Figure 7

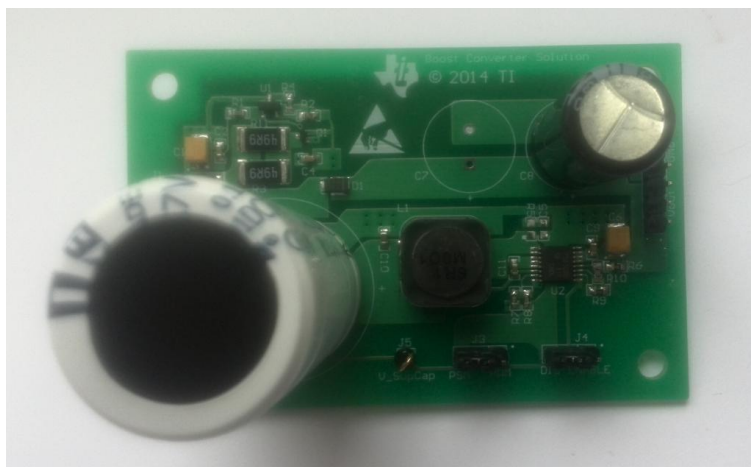


Figure 7: Reference Design Board

3 Bench Test Result

3.1 The Output Voltage after V_{SYS} Failure

A power supply Agilent E3634A is used to power the V_{sys} . The power supply is turned on and off to simulate the blackout and recovery of the grid.

The output voltage V_{out} before and after the grid failure at $I_{out}=100mA$ condition is showed in Figure 8, where CH1 is the supercap voltage V_{sup} ; CH2 is the boost converter output voltage V_{out} ; CH3 is the V_{sys} ; and CH4 is the SW pin voltage of TPS61030 V_{sw} .

When the V_{sys} voltage is at 5.3V, it supports the V_{out} through a Schottky diode and also charges the supercap, so the TPS61030 doesn't switch; when grid fails, the V_{sys} drops down. The boost converter starts switching to support V_{out} using energy in the supercap. It is observed from the waveform that the V_{out} keeps stable all the time.

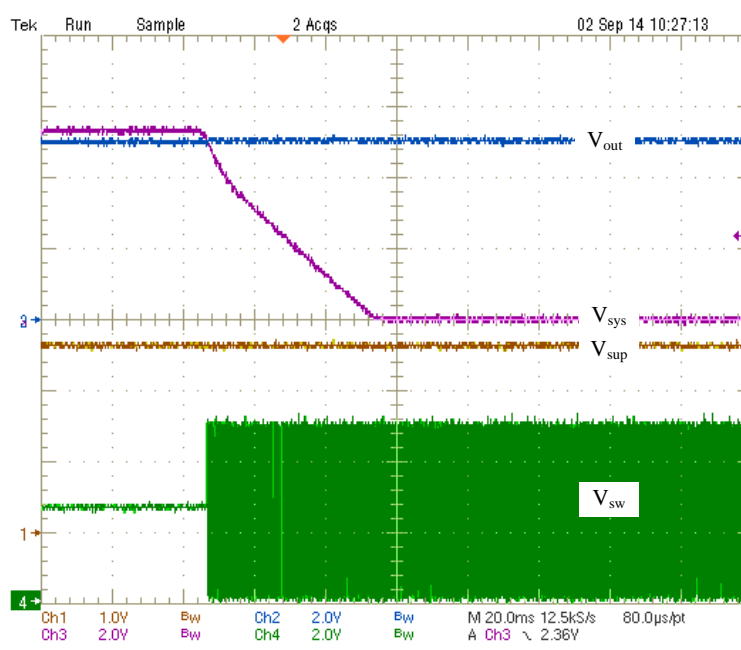


Figure 8: V_{out} at Grid Blackout

In Figure 9, the V_{sys} voltage returns to 5.3V to power the V_{out} , and the TPS61030 stop switching again. The V_{out} keeps stable in the transient period.

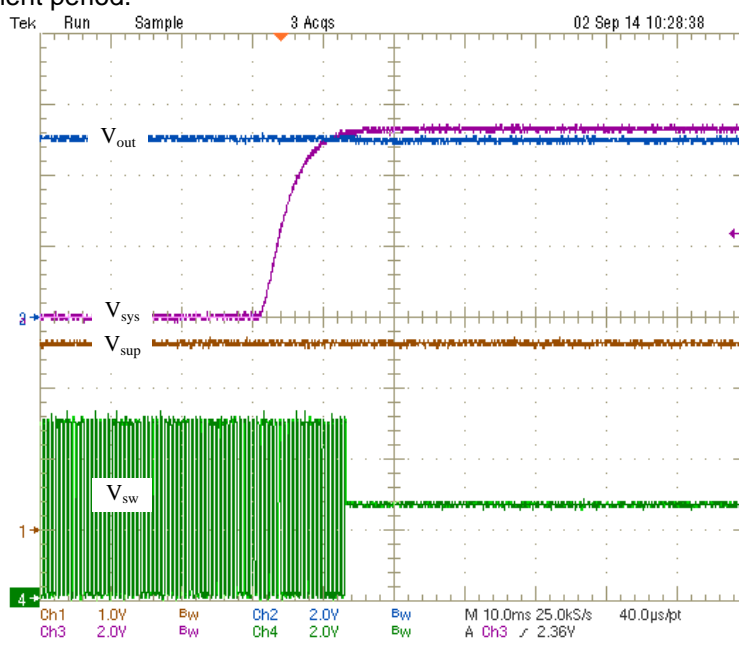


Figure 9: V_{out} at Grid Recovery

3.2 Output Voltage at GPRS Module Operating

Figure 10 shows the output voltage waveform at GPRS module operation when The V_{sys} voltage is normal. In the figure, I_{load} is the GPRS module current simulated by the resistor load. The V_{out} drops to 4.76V from 4.98V when $I_{load} = 2A$, and returns back to 4.98V if I_{load} comes to zero. The voltage under-shoot is mainly caused by the Schottky diode forward voltage at different current.

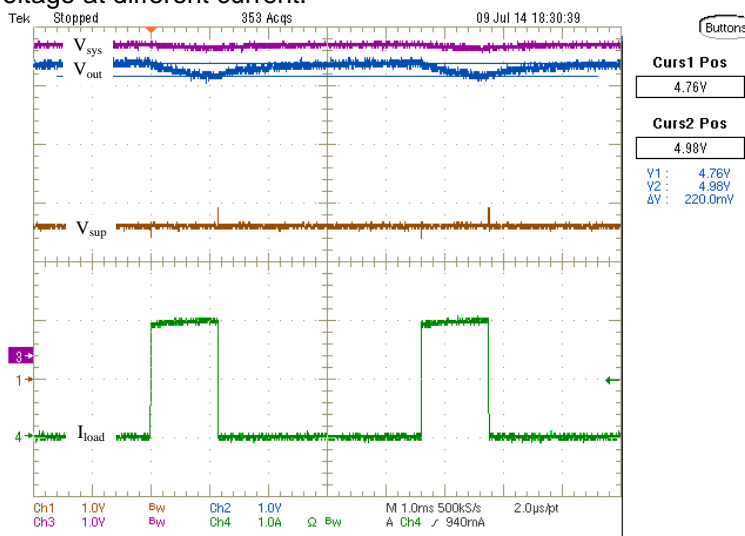


Figure 10: V_{out} at V_{sys} Voltage Normal

Figure 11 shows the V_{out} waveform when the V_{sys} fails and the GPRS module is still operating. The V_{out} is powered by the supercap, which is 2.6V at this condition. The under-shoot is only about 180mV, and the V_{out} keeps above 4.8V.

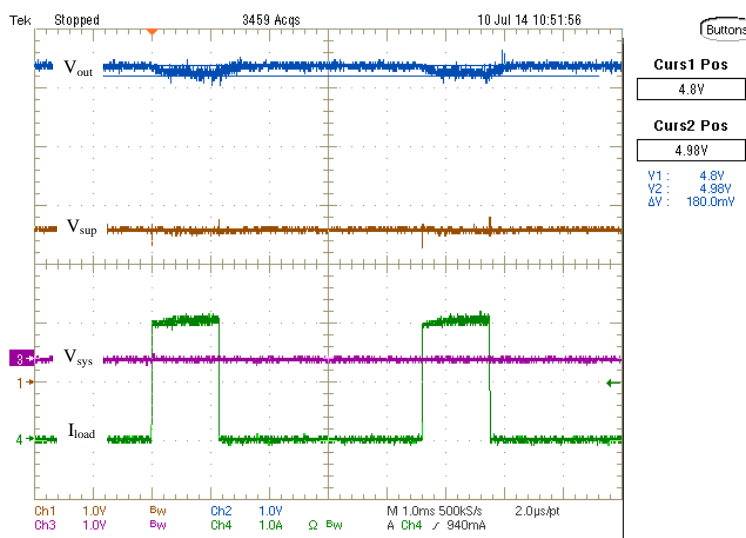


Figure 11: V_{out} Load Transient at $V_{sup}=2.6V$

The V_{out} switching frequency ripple at $I_{out}=2A$, $V_{sup}=2.6V$ condition is shown as Figure 12, where the $V_{out}(AC)$ is the output switching ripple. The peak-peak voltage ripple is about 136mV, which mainly be caused by the ESR of the tantalum capacitor and the aluminum capacitor.

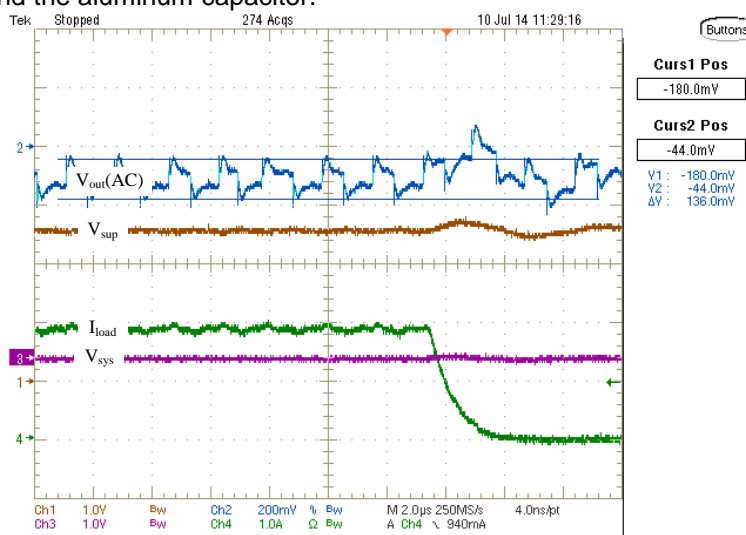


Figure 12: V_{out} Switching Ripple at $V_{sup}=2.6V$

Figure 13 and Figure 14 show the V_{out} load transient performance and output switching ripple at $V_{sup}=1.7V$ condition respectively. The V_{out} keeps between 4.98V and 4.72V and switching frequency ripple is about 140mV peak to peak.

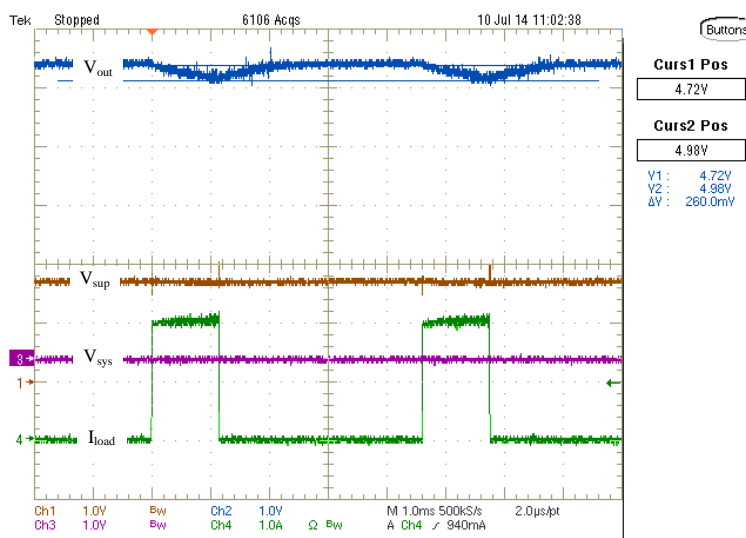


Figure 13: V_{out} Load Transient when $V_{sup}=1.7V$

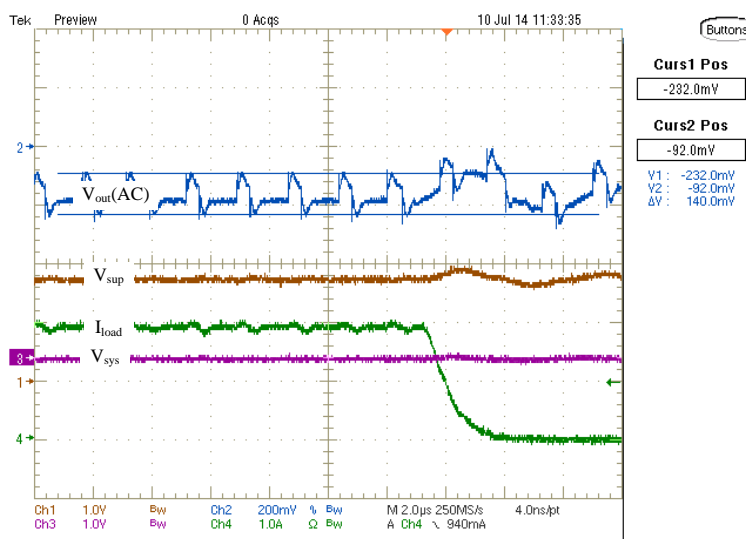


Figure 14: V_{out} Switching Ripple at $V_{sup}=1.7V$

3.3 Charging and Discharging the Supercap

The supercap charging curve from 0V to the targeted 2.65V is shown in Figure 15. It takes around 50 minutes to fully charge the supercap.

The supercap discharge curve when GPRS module operates is shown at Figure 16. The boost converter starts to power the load at $V_{sup}=2.64V$ and stop at $V_{sup}=1.65V$, which is the UVLO point of the TPS61030. The lasting time is 63s, which meets the design requirement but a little smaller than the expectation. One main reason is that some energy in the supercap can't be utilized when discharged fast.

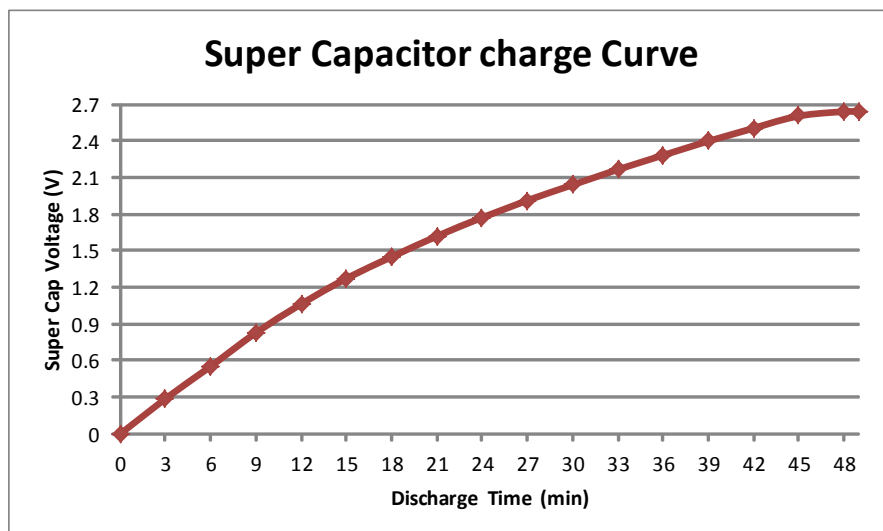


Figure 15: Supercap Charging Curve

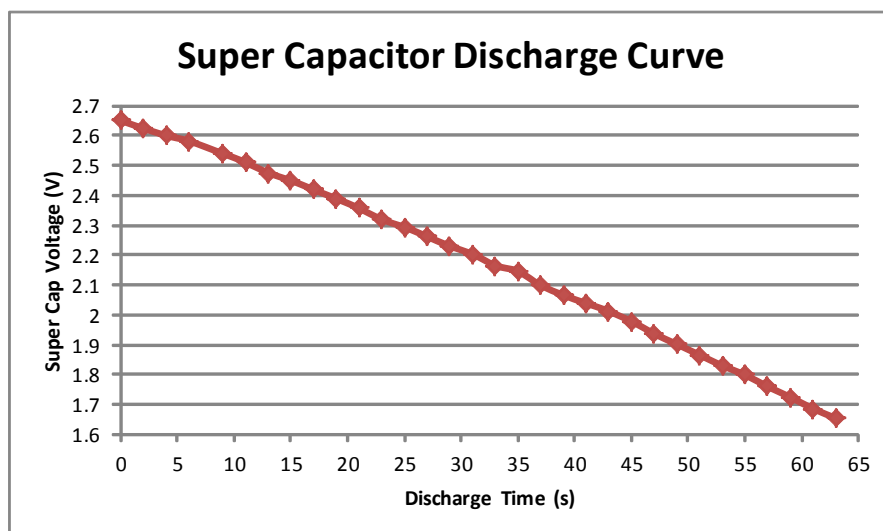


Figure 16: Supercap Discharge Curve

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.